



# CORTEX CENTRONICS INTERFACE

Any follow-up on the Cortex is long overdue, for which we apologise. We're now about to start setting this to rights.

The Cortex 16-bit computer was designed in late 1982 and was featured by ETI in the November 1982, December 1982 and January 1983 editions. It is based on the TMS9995 16-bit microprocessor with a full 64K byte main memory and a separate 16K byte memory for the colour graphics display. The machine can be expanded by simply adding chips to provide features such as floppy disc support and an expansion bus for extra memory, input and output. This article details how to use the EBUS bus expansion to plug an external board into your Cortex to provide a parallel data interface for a Centronics printer.

The E-BUS was developed to provide a compact, high-performance and flexible interface for both memory and input/output expansion. The E-BUS system multiplexes both addresses and data information onto its lines at different times, so as to keep the number of lines needed as low as possible. It can be shared by multiple microprocessors for access to common memory or I/O.

With regard to I/O expansion, some explanation of the computer's operation is necessary. When doing input and output operations, the CPU does not communicate in eight or 16-bit words, in contrast to most common processors which support dedicated I/O commands. Instead, the 9995 sends and receives just one bit at a time. This means that multi-bit input and output functions, like those needed for a Centronics printer for instance, have to be built up or broken down one bit at a time.

However, this operation is made simpler by the fact that each bit can be sent to or received from a unique address. So, to output eight bits to a peripheral, it is necessary to transfer the bits to a latch or similar device with eight successive single bit operations. Only then can the peripheral be told that the data is ready to be acted upon.

An input cycle occurs when the MEMEN (memory enable) control signal goes high (inactive); the bit address is output on the address/data bus and the single bit of data is sampled on the CRUIN signal. An output cycle is similar, except that the data bit is output on the CRUOUT signal and the CRUCLK control signal pulses active low. For multi-bit transfers, the cycle repeats with the address incrementing each time. A timing diagram for this is shown in Fig. 1.

During an I/O operation, the multiplexed address/data lines are forced to output the address

throughout the I/O cycle so no address latches are required, consequently the ALATCH (address latch) control signal remains high. The data bit to be sent appears as the signal CRUOUT on the least significant address line (A15 by the TI convention) when an output operation is performed. The remaining 15 address lines define 32768 addresses to which it can be sent, although the Cortex and the 9995 CPU use some of these addresses internally (see Fig. 2, the Cortex I/O map).

A data bit to be read in is taken via the CRUIN line. Up to 16 bits can be input or output by a single instruction, the specified number of bits being processed serially to or from the target addresses.

## The E-BUS

The kernel of the E-BUS interface on the Cortex is the 74LS-2001 gate array. This device is used to control access to the bus

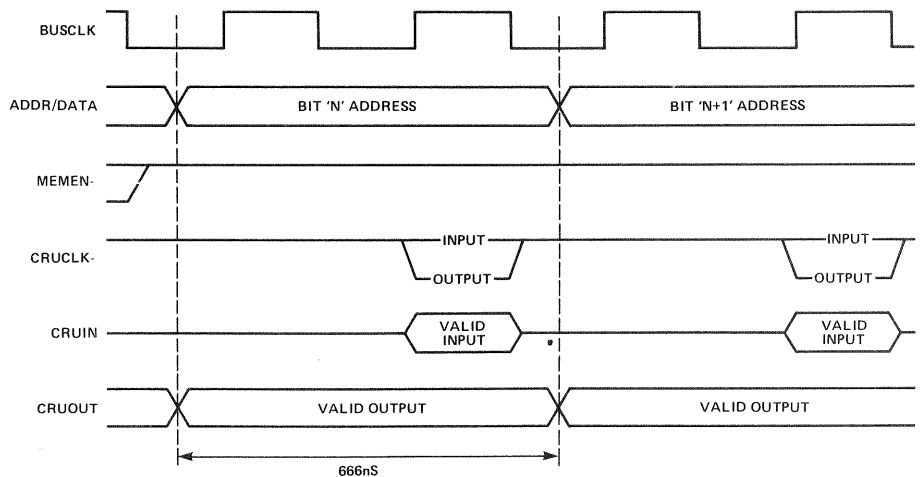


Fig. 1 Timing diagram for multi-bit transfers.

Address	Input Function	Output Function
0000	NOT USED*	"BASIC" LED
0002	NOT USED	KEYBOARD ACKNOWLEDGE
0004	DISK SIZE JUMPER	EBUS INTERRUPT ACK
0006	DISK DENSITY JUMPER	EBUS TIMEOUT ENABLE
0008	FLOPPY INTERRUPT FLAG	DISK SIZE
000A	KEYBOARD INTERRUPT FLAG	EPROM ON/OFF
000C	DISPLAY INTERRUPT FLAG	"BELL" ENABLE
000E	EBUS TIMEOUT INTERRUPT FLAG	NOT USED
0010 to 001E	KEYBOARD DATA	DUPLICATE OF ABOVE
0020 to 003E	DUPLICATE OF ABOVE	DUPLICATE OF ABOVE
0040 to 007E	NOT USED	NOT USED
0080 to 00BE	TMS 9902 RS232 PORT	TMS 9902 RS232 PORT
00C0 to 017E	NOT USED	NOT USED
0180 to 01BE	TMS 9902 CASSETTE PORT	TMS 9902 CASSETTE PORT
01C0 to 01FE	TMS 9911 DMA CONTROLLER	TMS 9911 DMA CONTROLLER
0200 to 07FE	external via EBUS	external via EBUS
0800 to 080E	external via EBUS	Centronics data via EBUS
0810	external via EBUS	Centronics strobe via EBUS
0812	Centronics status via EBUS	external via EBUS
0814 to 1EDE	external via EBUS	external via EBUS
1EE0	CPU internal	CPU internal timer control
1EE2	" "	" " timer interrupt enable
1EE4	" " level 1 interrupt flag	" " " "
1EE6	" " " 3 " "	" " " "
1EE8	" " " 4 " "	" " " "
1EEA	" " **	" " **
1EEC	" " ***	" " ***
1F00 to 1FD8	" " not used	" " not used
1FDA	CPU internal MID flag	CPU internal
1FDC to 1FFE	external via EBUS	external via EBUS

\* Some systems may have this used for floppy disk interface  
 \*\* Cortex Basic uses this bit to enable the display on the TV screen of all control characters.  
 \*\*\* Cortex Basic uses this bit to disable the scrolling of a text display on the TV screen.

for multiple microprocessors and to synchronise all data transfers, as well as to provide time-out controls to avoid a permanent lock-up of the bus. However, for simple expansion of the Cortex facilities, it is possible to avoid using this device. Four changes to the main PCB have to be made, as follows:

1. Cut the connection to IC99 pin 18 and connect this pin to IC94 pin 11;
2. Connect IC94 pin 9 to IC11 pin 13;
3. Connect IC94 pin 19 to IC27 pin 2;
4. Connect IC89 pin 18 to IC89 pin 19.

For this modification to work, the

## HOW IT WORKS

IC1a, IC1b and IC2 decode address bits A4 to A11 inclusive. Two outputs from IC2 are used each of which will go low when one of their particular group of eight addresses is accessed. Note that the address decoding is not complete and may well respond at other locations (2K interval). The Y1 output from IC2 (address 0088h to 008Fh) enables the output of IC4 (74LS251) the 1 of 8 selector. This device selects the signal on the input specified by the least significant address lines and passes it to the CRUIN line. This would normally be the printer status line in this case and its state will signal whether the printer is ready to receive data.


The data to be output to the printer appears on the CRUOUT line in serial form. This has to be converted to parallel form before being presented to the printer. This is done by IC3 which is an eight bit addressable latch (74LS259). Address lines A12, 13 and 14 determine which bit is to be written into IC3 and the output Y0 of IC2 gated with CRUCLK in IC1d actually causes it to happen. To write a complete eight bits of new data requires eight output cycles. Once this has been done the data is ready to be acted upon by the printer. IC5 is another 74LS259 like IC3 and one bit of its output is used as a strobe signal to tell the printer that the data is ready. Output Q0 is used in this case; it is normally low and is pulsed high under software control. This happens when a 1 and then a 0 is output to 0088h.

For the transfer of one character the sequence is as follows: eight bits of data are written into the eight locations in IC3. The data then appears in parallel form at its output and is available to the printer. The DATA STROBE is taken high and then low to signal to the printer that valid data is ready. The printer signals that it is BUSY by taking the BUSY STATUS line high. This is read by the computer and no further action is taken until it goes low again. Now new data can be sent to IC3 and the process repeated.

Note that some printers give a low on the status line to indicate the BUSY condition, this can be accommodated by connecting the EBUS CRUIN line to IC4 pin 6 instead of pin 5. More difficult is when the STROBE has to be inverted, this requires an additional inverter.

Fig. 2 (above) Cortex I/O map.

Fig. 3 Interface circuit.

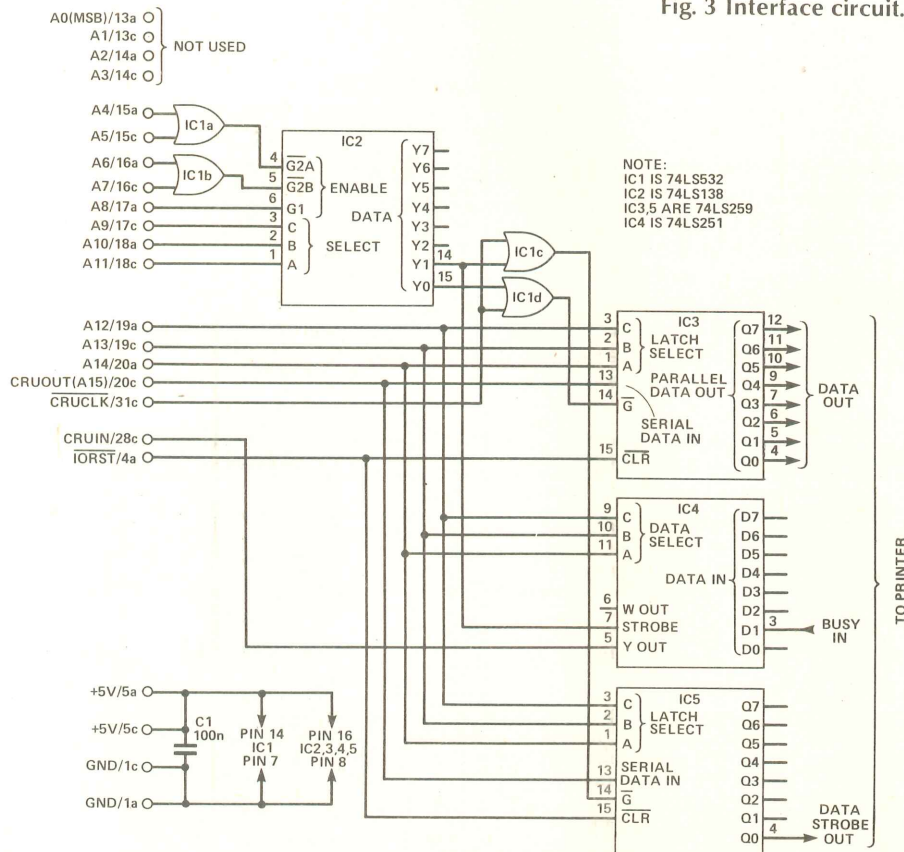

# PROJECT : Cortex Centronics

following devices must be present on the PCB (if your Cortex does not have all the options available, then some of these may be missing, so you will need to check): IC90 (74LS08), IC91 (74LS32), IC92 (74LS74A), IC93 (74LS00), IC94,95,96 and 99 (all 74LS244).

If you wish to use memory expansion, then you must break the links next to IC26 and drill out the shorting links next to IC94, and ensure that you have IC97 (74LS245) and IC26 (74LS612). Note that all the component numbers used here are those given in the original Cortex article.

## It's Already There

Although the Cortex has an RS232 interface for a printer or terminal, it also has the software necessary to drive a parallel data printer port. The hardware necessary to implement this was left off the main PCB to save space. Building the interface described here will therefore free the RS232 for other tasks, and make it possible to use the more common Centronics printers.

The circuit diagram for the

I/O	ROW A	PIN	ROW C	I/O
	GND 0V	1	GND 0V	
I/O	PRES- (RESET-)	2	BUSCLK (3MHz)	O
	+12V	3	-12V	
O	IORST- (I/O RESET-)	4	NMI-(NON-MASKABLE INT)	I
	+5V	5	+5V	
	—	6	—	
	—	7	—	
	—	8	—	
	—	9	—	
I	INTEN- (LEVEL 1)	10	ALATCH (ADDRESS LATCH)	O
O	XA0 (MSB ADDRESS)	11	XA1	O
O	XA2	12	XA3	O
O	A0	13	A1	O
O	A2	14	A3	O
O	A4	15	A5	O
O	A6	16	A7	O
I/O	A8/D8 (DATA MSB)	17	A9/D9	I/O
I/O	A10/D10	18	A11/D11	I/O
I/O	A12/D12	19	A13/D13	I/O
I/O	A14/D14	20	A15/D15/CRUOUT (LSB)	I/O
	—	21	MEMEN- (MEMORY ENABLE)	O
O	DEN- (MEMORY READ)	22	READY- (MEMORY READY)	I
I	GRANTIN	23	GRANTOUT	O
	—	24	BUSY- (BUS BUSY)	I/O
	GND	25	GND	
	—	26	—	
	—	27	—	
	—	28	CRUIN (I/O INPUT)	I
O	WE- (MEMORY WRITE)	29	—	
	+5V	30	+5V	
	—	31	CRUCLK (I/O WRITE STROBE)	O
	GND	32	GND	

Fig. 4 EBUS signals and their uses.

interface is shown in Fig. 3 and the circuit itself is discussed in the 'How It Works' section.


Next month we will publish the PCB, overlay, parts list and buy-lines.

ETI

## FOR HI-FI & ELECTRONICS ENTHUSIASTS CONCEPT ELECTRONICS LTD 51 Tollington Road, London N7 6PB

Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

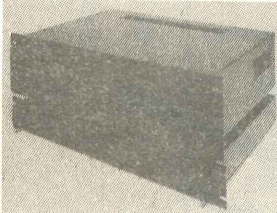Professional rack mounting cabinet	Panel Size		Rear Box		Price	
	W	H (inch)	W	H	AL	STEEL
	19	5	17 x 4.5	10	27.54	23.54
	19	4	17 x 3.5	10	25.24	21.24
	19	3.5	17 x 3	10	24.09	20.09
	19	3	17 x 2.5	10	24.09	—
	19	2.5	17 x 2	10	22.94	18.94
	19	6	17 x 5.5	12	28.69	24.69
	19	5	17 x 4.5	12	27.54	23.54
	19	4	17 x 3.5	12	25.24	21.24
	19	3.5	17 x 3	12	24.09	20.09
	17	3.5	15.5 x 3	9	21.79	17.79
	17	2.5	15.5 x 2	9	20.64	16.64
	17	4	15.5 x 3.5	12	25.24	21.24
17	3	15.5 x 2.5	12	24.09	20.09	

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access ★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.


The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

### CONTROL MODULES



- TY-7 Electronic touch switch  
£2.90 Kit £4.50 Ass.
- TY-11 Light activated switch  
£2.20 Kit £3.50 Ass.
- TY-18 Sound activated switch (Clap switch)  
£4.50 Kit £5.95 Ass.
- TY-38 Sound activated switch (voice-switch)  
£5.50 Kit £7.50 Ass.
- TY-41 Infra-red remote control (Receiver and transmitter)  
£17.20 Kit £21.95 Ass.

### HI-FI AMPLIFIER MODULES

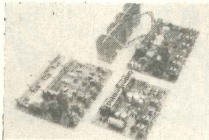

- TA-323A 30W + 30W stereo amplifier  
£18.95 Kit £23.95 Ass.
- TA-820 60W + 60W stereo amplifier  
£27.50 Kit £33.50 Ass.
- TA-920 70W + 70W stereo amplifier  
£35.50 Kit £42.50 Ass.

# KITS FROM £7 ...TO £60

## Sparkrite

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form – And save pounds!!

- Electronic Ignition systems – contact triggered and contactless
- Electronic Car Security Systems – including a new ultrasonic unit
- Car Drive Computer – with 12 functions

SEND FOR FREE LITERATURE PACK – TODAY!

8 SOPHISTICATED  
KITS TO CHOOSE  
FROM.

To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.  
Telephone: 01-804 4343

NAME .....

ADDRESS .....

ETI