

PO Box 149,
Pennant Hills,
N.S.W. 2120
(02)8480956

Volume 1, Number 1.

In this TECHNO-SHEET, we'll look at making up 3 items of interest to many of our members around Australia.

The first being your very own, hand made LIGHT PEN;

The second being WIRING UP YOUR ACOUSTIC COUPLER LEAD;

And the third, converting the ATARI JOYSTICKS for the 99/4 & 4A



So let's start with the LIGHT PEN...first you'll need the following parts:-

- (1) 9-PIN "D" CONNECTOR
- (2) RG 174/U COAXIAL CABLE
- (3) DA 20961 SHIELD
- (4) FELT-TIP or BALL POINT PEN CASE
- (5) 470 K-OHM RESISTOR
- (6) 47 K-OHM RESISTOR
- (7) .047uf CAPACITOR
- (8) TIL404 TRANSISTOR
- (9) 2N2907 TRANSISTOR

The photo-transistor (TIL404) is connected to one end of the wire and inserted into the pen case.

It can be held in place by silicone glue about 5 to 10mm from the end of the pen.

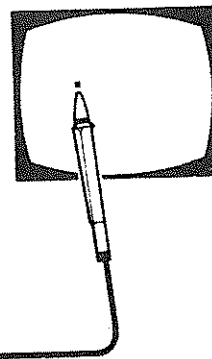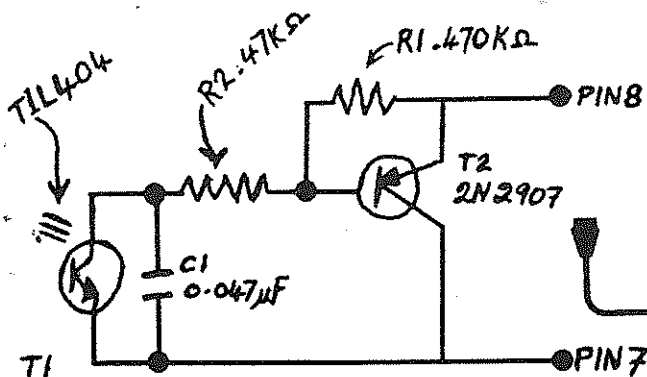The rest of the components can be connected together just before the joystick connector. It is added by using pins 8 & 7.



309
270
Fick
290
79d
139


10
1E

ACOUSTIC COUPLER & RS 232 INTERFACE

Before you attempt to connect your computer to OTC's SATELLITE, for communication with THE SOURCE, & TEXNET etc...there are a few things you will need.

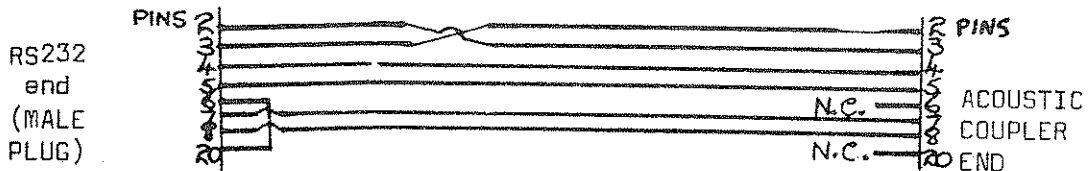
- (1)RS 232 INTERFACE, (2)ACOUSTIC COUPLER or Telecom Modem,
- (3)MIDAS A/c(Application form from OTC in your state),
- (4)SOURCE A/c(Contact us for more information on this.)
- (5)CHARGE A/c(i.e. Overseas Bankcard= Visa/MasterCharge/Amer.Express)
- (6)TERMINAL EMULATOR MODULE(preferably the TE2

Although the RS 232 Interface & Acoustic Coupler(DSE Cat. X-3270 or Electro.Med of Victoria "SENDATA MODEL 700") are RS 232c standard, they are not immediately compatible. This problem can be overcome by using an adapter cable wired as shown below, or you may obtain one ready made from the Brisbane User Group.



JOYSTICK CONVERSION

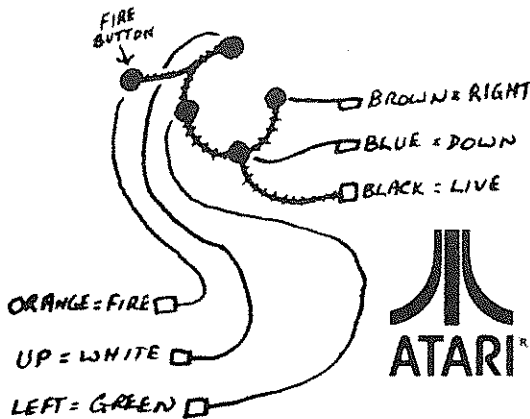For those who have the TI Joysticks & wish to wire up to ATARI Joyst Cases.
ATARI PCB...



the TI-99/4

FIRE = BLACK
UP = ORANGE
LEFT = BROWN


BLUE = RIGHT
GREEN = DOWN
WHITE = LIVE

So now you can use the 'Y' lead from the TI Joyst's. You will now notice that all motion on screen will be smooth & the Joysticks fun to use... HOWEVER:::when you try to move diagonal(both at the same time)all motion will slow to stop. You then have to remove the Diodes from the PCB tracks of the TI, and place them on the same tracks of the ATARI ones. This can be done simply by drilling two small holes in each track, and cutting the track between the two holes before soldering the Diodes in. MAKE SURE YOU PUT THE DIODES IN THE RIGHT DIRECTION.

If you have not already bought TI Joyst, there is no need for you to do so. You can make the ATARI joysticks work on the TI with the following modification.


All you need is two ATARI Joysts, available from most Atari distributors, ten 1n4001 diodes, available from any electronic component shops, one 9 pin plug & case, you can use one of the plugs on the Atari Joyst as an example, you can also get this plug from Martin DeLauney.

Your first step is to solder in the diodes, which can be done in one or two ways, either solder them in the p.c.b. track of the Atari joysts, you need to drill two small holes in every track EXCEPT the track off the black lead where no diode is required here, cut the solder between the two holes in each track so as to make a bridge, then insert the diodes in each track, making sure to point the cathode toward the joystick, this is important, otherwise the joysts will not work.

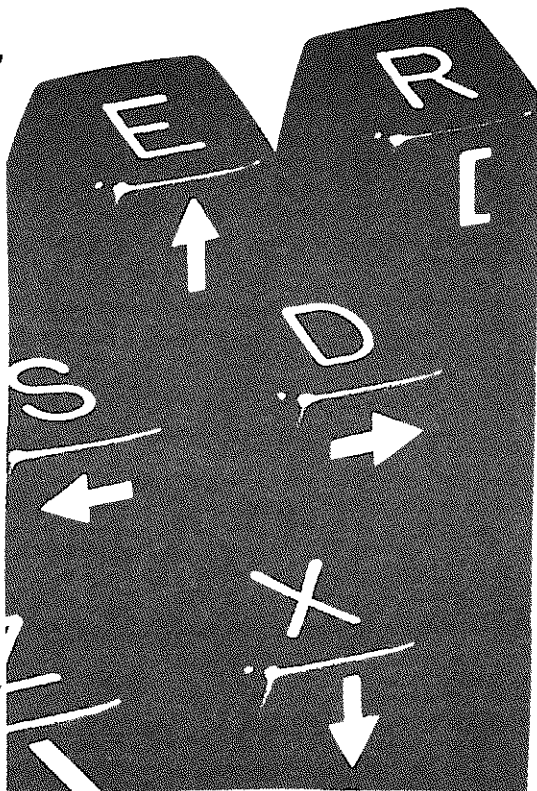


Then solder the diodes in, (you must do this on BOTH joysts). THE SECOND WAY:- is to cut each wire off the joystick, (except the black wire), cut the wire about $\frac{3}{4}$ " away from the clip off the PCB then cut the wires of the diodes about $\frac{3}{16}$ " from each side off the body of the diodes, and solder the diodes in line straight to the wires, remembering to point the cathode toward the clips, then put a strip of insulation tape around each diode, making sure to cover the naked wires. Screw back the joysts neatly.

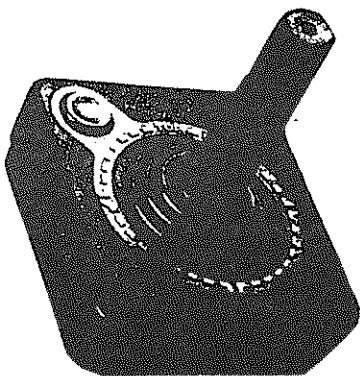Both methods were tried and tested, successfully. The NEXT STEP IS:- to solder your plug together, firstly cut off the Atari plugs and discard them, if you wish. You must now solder the wires on both joysts together, that is: white lead to white lead, orange lead to orange lead etc.



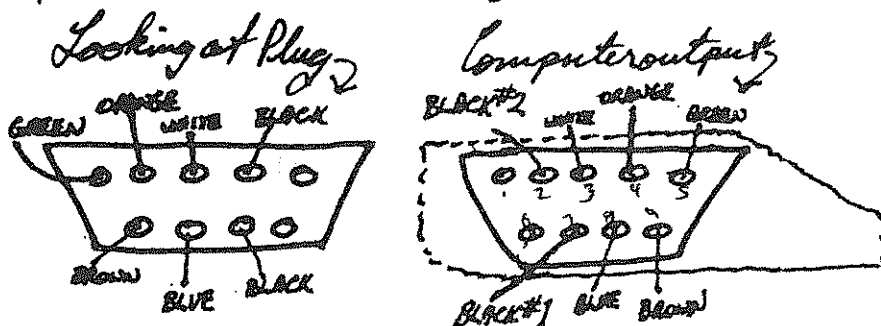Do this to all colours except BLACK, these must stay separate. You can please yourself how you connect the plug together, but you must put the right colour wire to the right pinhole as shown on this diagram...



I suggest that before you solder your joined wires to the pins, that you solder one inch of wire to each join, making a Y shaped union, this will make it easier for you to solder on the pins.

Before you put your plug together, remember to put some insulation tape around all naked wires. Now put the plug together, and you're in business, get out your soccer module with a friend, and I guarantee you won't be able to tear yourself away from them.

If it doesn't work...check all your soldering for good connections, and check that no wires are touching, and that you have all the diodes facing the right way plus the correct wire combinations are as explained in this report.

